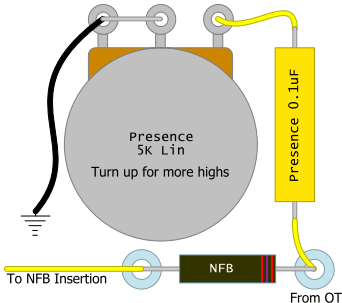


# Presence Control



The Presence Control Circuit removes high frequencies from the NFB Circuit which boosts highs at the speaker.