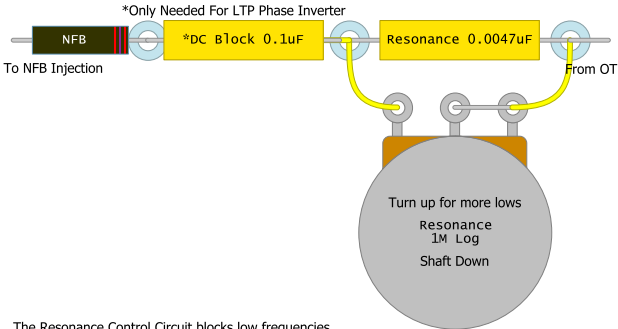


Resonance Control



The Resonance Control Circuit blocks low frequencies in the NFB Circuit which boosts lows at the speaker. For best results put the Resonance Control on the output transformer side of the NFB Resistor.